

AN002**Optimising CC400/CC900/CC1000 for low LO leakage**

By P. M. Evjen and S. Vetti

Keywords

- Minimising LO leakage
- RX spurious emission
- PCB reference designs
- EN 300 220 requirements
- Type approval
- Power decoupling

Introduction

The ETSI standard for license-free short range devices (SRDs) in the 433/868 MHz bands, EN 300 220, sets the requirement to receiver spurious emission to <-57 dBm. FCC (USA) has similar, but somewhat less strict regulations. This application note deals with LO leakage in detail. This includes findings from making numerous of reference designs. Chipcon

has reference designs for all our transceivers. LO leakage is the single most important reason for users of the CC400/900/1000 to **copy** these layouts/BOM to the **smallest detail**. The requirement for an LO leakage of -57 dBm is met for all our reference designs.

Overview

In order to optimise a CC400/CC900/CC1000 design and layout for low spurious emission there are three critical factors. The first is the VCO amplitude set by the VCO current, the second is the “air” coupling from the VCO tank to the output matching network and the third is the coupling through the different internal power supplies (example: VCO to LNA power supply).

The VCO current can be controlled and reduced to a minimum level for appropriate operation. For CC400/900 the current is controlled by a 3-bit word in register location C[11:9]. Maximum current is achieved for C11:9=[000], minimum current is given by C11:9=[111]. The VCO current is less important for CC1000 with respect to LO leakage (use the SmartRF Studio default)

The coupling between the VCO tank and the matching network at the output is dominated by the inductive coupling

between the VCO tank inductor, and the TX and RX match inductors. It is important to minimise this coupling in order to reduce the spurious emission. This is done by the using the optimal inductors with the optimal orientation in combination with the optimal layout (see below).

The coupling through the power supplies (VCO power to the LNA power) can be reduced with a correct decoupling of the VCO power to GND. It is important to realise that the decoupling frequency is high (RF) when choosing the value of the capacitor and the PCB placement. The value of this decoupling capacitor could be as low as 12 pF for 868 MHz and 33 pF for 433 MHz. Inductor types and orientation will also effect the LO leakage coupling to the different power sets. Use the inductors suggested by Chipcon, at least as a starting point, and use the same orientation!

Reducing LO leakage for CC400/CC900

CC400 and CC900 are somewhat equal, however they do not have the same pin-out. The most important difference with respect to LO leakage is the different power pins for the VCO and the LNA/PA.

Table 1 Different VDD pins for CC400/CC900

	PIN NUMBER CC400	PIN NUMBER CC900
VCO_VDD	8	9
LNA_PA_VDD	7	8
VCO_GND	10	11 (also GND for the prescaler)
LNA_PA_GND	4	4 and 5

Reducing the VCO-to-matching network coupling (CC400/CC900)

The CC400/900 Demonstration Board is equipped with inductors manufactured by Murata, type LQW2BH/LQN21A Series (AirCore-Wound type). These are wound in the vertical direction (same way as you would wind a coil around your thumb with the thumb sticking upwards). Rotating these coils 180 degrees, results in a phase inversion of the radiated field.

It has been found through testing that for this layout and this particular type of inductors the optimum orientation is as shown Figure 1 in below. Note the orientation of the inductor, illustrated by on which side of the inductor the wire is terminated. L91 is the VCO inductor, while L61 and L51 is part of the output/input network. Note that L91 also influences the coupling to the different power supplies.

Shielding the VCO tank circuit will reduce the LO leakage by about 3 dB. The shielding will also reduce noise (for example GSM) coupling into the VCO, so shielding is highly recommended (CC400/CC900).

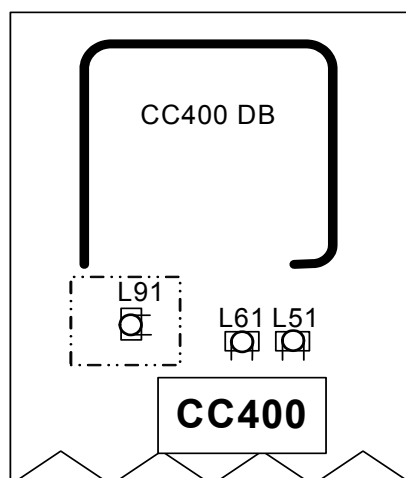


Figure 1

Adjusting the VCO current (CC400 and CC900)

The VCO current is controlled by a 3-bit word located in register bits C[11:9]. Maximum current is achieved for [000], and minimum current for [111].

In TX mode the [000] setting is suggested used (if low phase noise is important, a lower current setting should be investigated). In RX mode the current can be reduced in order to reduce the amplitude in the VCO tank and hence the leakage. Using the CC400DB, Demonstration Board the current is set to [100] for optimum performance, giving adequate LO suppression and current margin, this also gives the best sensitivity. For your design: Verify that the VCO starts up for temperature and VDD extremes. Note that lower VCO current than 100 is not recommended and might prevent the VCO from starting up in worst-case conditions. For inductors with lower Q than the LQW2BH/LQN21A Series (not recommended), a higher VCO current might be needed.

Decoupling of the individual VDD power supplies (CC400/CC900)

The most important pin to decouple is the VCO power supply pin, see table 1 (CC400 and CC900 are different). The optimised decoupling capacitor value is depending on the frequency and is rather small compared to “normal” decoupling capacitor values. The reason for this is that the total pin/pcb/via inductance and the decoupling capacitor forms a series resonant circuit that will give a very low impedance path to ground when it resonates at the RF frequency of interest. For the CC400 reference design (CC400DB, Demonstration Board), this capacitor is C24 = 33pF (RF = 433 MHz). For the CC900 reference design (CC900DB Demonstration Board), this capacitor is C25 = 12pF (RF = 868 MHz).

Note that the decoupling capacitor should be placed as closed as possible to the chip to keep the wires as short as possible. If possible, more than one via should be used to reduce the lead inductance.

Reducing LO leakage for CC1000

All the coupling mechanism mentioned above is also valid for CC1000. If the suggested KOA inductor is used, the LO leakage is well below the -57dBm requirement (for Europe). The KOA inductor is a thin film high Q chip inductor (0805) on a ceramic substrate. Note that the orientation is VERY important for the KOA inductor, the LO leakage will increase by 20-30dB if the orientation is “wrong”. See the CC1000 Plug and Play module for a reference design.

Reference Designs (Layout/BOM)

For CC400 : CC400DB, Demonstration Board

For CC900 : CC900DB, Demonstration Board

For CC1000 : CC1000PP, Plug and Play module

Note that the CC1000 Development Kit includes 2 CC1000PP Plug and Play modules.
See www.chipcon.com for Gerber and BOM.

Conclusion

Sufficient LO suppression ($<-57\text{dBm}$) can be achieved for all Chipcon transceivers, copy the reference designs !

This application note is written by the staff of Chipcon to the courtesy of our customers. Chipcon is a world-wide distributor of integrated radio transceiver chips. For further information on the products from Chipcon please contact us or visit our web site.

Contact Information**Address:**

Chipcon AS
Gaustadalléen 21
N-0349 Oslo,
NORWAY

Telephone	:	(+47) 22 95 85 44
Fax	:	(+47) 22 95 85 46
E-mail	:	wireless@chipcon.com
Web site	:	http://www.chipcon.com

Disclaimer

Chipcon AS believes the furnished information is correct and accurate at the time of this printing. However, Chipcon AS reserves the right to make changes to this application note without notice. Chipcon AS does not assume any responsibility for the use of the described information. Please refer to Chipcon's web site for the latest update.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DSP	dsp.ti.com	Broadband	www.ti.com/broadband
Interface	interface.ti.com	Digital Control	www.ti.com/digitalcontrol
Logic	logic.ti.com	Military	www.ti.com/military
Power Mgmt	power.ti.com	Optical Networking	www.ti.com/opticalnetwork
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
		Telephony	www.ti.com/telephony
		Video & Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments
Post Office Box 655303 Dallas, Texas 75265

Copyright © 2006, Texas Instruments Incorporated